# **Report of Assignment 4**

Ang, Chen 118010009

The Chinese University of Hong Kong, Shenzhen

### Introduction

In this project, we implemented a 5-stage (5 clock cycles) pipeline MIPS architecture processor using Verilog HDL. The CPU contains 8 general registers and supports 26 basic MIPS instructions via ALU. Data can be transferred in and out of the simulated memory and the general registers. Branch/jump of instructions are supported via management of PC. This CPU does not handle any pipeline hazard.

## **Five Stages**

The five stages of the the pipeline CPU are:

- 1. Fetch
  - (1) PC updated
  - (2) New instruction fetched from instruction memory at PC
- 2. Decode
  - (1) Instruction split and decoded by the control unit
  - (2) Sign extension
- 3. Execute
  - (1) ALU executes the operation
- 4. Memory I/O
- 5. Writeback
  - (1) Result written back into the register file

# **Block Diagram**

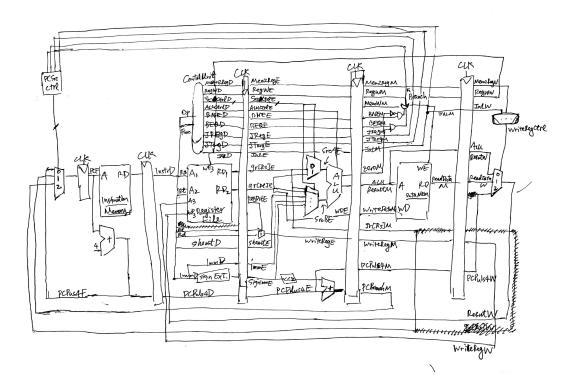


Fig. 1. Block diagram of the MIPS architecture processor without hazard handling

# **Implementation Details**

### **Pipelining**

The pipeling behavior of the CPU is implemented via writing sequential logic in Verilog. Specifically, each control signal CS is treated as a vector with entries corresponding to the stages in which the signal is used for. And we used the always block to advance the signals as follows:

```
always @(posedge CLK) begin
    CS[1] <= CS[0];
    CS[2] <= CS[1];
    CS[3] <= CS[2];
    //...
end</pre>
```

Logic within each stage is purely combinational and they are put in a separate always block, for example:

```
always @(*) begin
   PCPlus4[0] = PC + 4;
   PCBranch[0] = PCPlus4[2] + (signImm[1] << 2);
   opcode = instr[31 : 26];
   funct = instr[05 : 00];
   //...
end</pre>
```

### Memory and Register I/O

Both data/instruction memory and eight general registers are implemented as Verilog regs:

```
// MEMORY I/O
reg[31 : 0] dataMemory[10000:0];
reg[31 : 0] instrMemory[1000:0];
// REGISTER I/O
reg[31 : 0] gr[7:0];
```

Then both memory and registers can be accessed using indices. One thing worth noting is that dataMemory/instrMemory should not be accessed directly via the address as it is treated as a 32-bit reg (rather than byte-indexed). Therefore we must divide the address by four to obtain the correct index of the desired word in dataMemory/instrMemory.

In the Fetch stage, instructions are fetched for decoding through

```
instr = instrMemory[PC / 4];
```

Using rs, rt from the split instruction we can read data stored in the registers:

```
gr[rs]; gr[rt];
```

In the Memory stage, data can be pulled out:

```
readData = dataMemory[ALUResult / 4];
```

or written into dataMemory:

```
If (memWrite) dataMemory[ALUResult / 4] = writeData;
```

Finally in the Writeback stage, the result can be written back to register file:

```
if (regWrite) gr[writeReg] = result;
```

#### **Control Unit**

The control unit processes the opcode and function codes during the Decode stage which would eventually tell the ALU which operation to perform through ALUctrl. Other control signals are generated as well, including

- srcActrl/srcBctrl(0~4), which determine the source of operand A/B;
- branchEQ & branchNE, which, combined with ZeroFlag, control loading branch target into PC.
- JReg/JTarg, which control the source of the jump target;
- memToReg/Jal, which determine data source to be written into the register;
- memWrite/regWrite, which enables data write into memory/register;
- regDst, which determines the destination register to write data into.

These signals are generated within the case block (upon the opcode and function code of the instruction) of Verilog. Some of the control signals of each instruction are shown below.

Instr	Operation	ALUctrl	srcActrl	srcBctrl	regDst
add	+	0	rs (1)	rt (0)	rd (1)
addu					
addi				signImm (3)	
addiu					rt (0)
lw					110 (0)
SW					
sub	-	1		rt (0)	rd (1)
subu					ru (1)
beq					
bne					x
and	&	2			
andi				imm (2)	rt (0)
nor	~	3		rt (0)	rd (1)
or	I	4			
ori				imm (2)	rt (0)
xor	۸	5		rt (0)	rd (1)
xori				imm (2)	rt (0)
slt	slt (±)	6		rt (0)	
slti					rd (1)
sltu	slt (∅)	7			Tu (1)
sltiu					

s11	<<	8	rt (0)	shamt (4)	
sllv				rs (1)	
srl	<b>&gt;&gt;</b>	9		shamt (4)	
srlv				rs (1)	
sra	<b>&gt;&gt;&gt;</b>	10		shamt (4)	
srav				rs (1)	

±: signed; ∅: unsigned

Table 1. Grouping of supported instructions by operations(ALUctrl.) srcA, srcB, regDst and their encoding listed.

#### **Main ALU**

The main ALU conducts the operation encodes by ALUctrl on two input operands. Thus ALU needs to first decode the ALUctrl. This decoding is again realized using the case instruction. What remains is to simply to tell the ALU to conduct the basic operations listed above as most of these binary operations are built into the Verilog. Some operations among them do need to be distinguished between signed and unsigned versions, while *regular operators in Verilog are by default unsigned*. Luckily the Verilog has an built-in function \$signed() which handles this scenario for us. By directly converting both operands a, b into \$signed(a) and \$signed(b), any operation X on them will automatically become signed as well. Another type of operation worth mentioning is the shifting. Sometimes when the shift amount is indicated by a register as in sllv or srav, the amount for shifting could be too wide (>32) and cause an error. This is handled by reducing the shift amount modulo 32, or equivalently, anding it with 0x1F, which prevents undefined shifting behavior.

# **Branch and Jump (PC management)**

PC is updated at each clock either to PCP1us4 from stage F (in normal cases), or PCBranch from stage M (for successful branches), which is

```
PCBranch = PCPlus4 + (signImm << 2);</pre>
```

or PCReg from stage M (for jr), or PCTarg from stage M (for j and jal). The source of the PC is controlled by three control signals: branchCtrl, jumpReg, and jumpTarg. The branchCtrl indicates a successful branching condition, namely,

branchCtrl = (branchEq & zeroFlag) | (branchNE & !zeroFlag);

enabling the source PCBranch. (Otherwise it would be normal increment of PC by 4). For jump instructions, jumpReg and jumpTarg enables PCReg and PCTarg, respectively.

### **Examples**

#### Input:

```
// Data Memory
uut.dataMemory[0] = 32'h0000_00ab; // address 0x00
uut.dataMemory[1] = 32'h0000_3c00; // address 0x04
// Instruction Memory
uut.instrMemory[0] = {6'b100011, `gr0, `gr1, 16'h0000}; // lw gr1, gr0(0)
                                                                  (gr1 <= memorv[0x00])
uut.instrMemory[2] = {6'b101011, `gr0, `gr0, 16'h0008}; // sw gr0, gr0(8)
                                                                    (data[0x08] <= 0)
uut.instrMemory[4] = {6'b001001, `gr0, `gr3, 16'h0002}; // addiu gr3, gr0, 2 (gr3 <= 0 + 2)
uut.instrMemory[5] = {6'b000000, `gr1, `gr2, `gr3, 5'b00000, 6'b100000}; // add gr3, gr1, gr2 (gr3 <= gr1 + gr2)
uut.instrMemory[6] = {6'b000000, `gr1, `gr2, `gr3, 5'b00000, 6'b100010}; // sub gr3, gr1, gr2 (gr3 <= gr1 - gr2)
uut.instrMemory[7] = {6'b000000, `gr1, `gr2, `gr3, 5'b00000, 6'b100001}; // addu gr3, gr1, gr2 (gr3 <= gr1 + gr2)
 uut.instrMemory[8] = \{6'b000000, \ gr1, \ gr2, \ gr3, \ 5'b00000, \ 6'b100011\}; \ // \ subu \ gr3, \ gr1, \ gr2 \ (gr3 <= \ gr1 - \ gr2) \} 
 uut.instrMemory[10] = \{6'b000000, `gr1, `gr2, `gr3, 5'b00000, 6'b100101\}; \ // \ or \ gr3, \ gr1, \ gr2 \ (gr3 <= \ gr1 \ | \ gr2) \} 
uut.instrMemory[11] = {6'b000000, `gr1, `gr2, `gr3, 5'b00000, 6'b100111}; // nor gr3, gr1, gr2 (gr3 <= gr1 ~| gr2)
uut.instrMemory[12] = {6'b000000, `gr1, `gr2, `gr3, 5'b00000, 6'b100110}; // xor gr3, gr1, gr2 (gr3 <= gr1 ^ gr2)
 uut.instrMemory[13] = \{6'b001100, `gr0, `gr0, `gr3, 16'h1111\}; \quad // \ andi \ gr3, \ gr0, \ 0x1111 \quad (gr3 <= 0 \ \& \ 0x1111) \} 
uut.instrMemory[14] = {6'b001101, `gr0, `gr3, 16'h1111}; // ori gr3, gr0, 0x1111 (gr3 <= 0 | 0x1111)
 uut.instrMemory[15] = \{6'b000000, `gr0, `gr1, `gr3, 5'b00001, 6'b000000\}; \ // \ sll \ gr3, \ gr1, \ 1 \ (gr3 <= \ gr1 << 1) 
uut.instrMemory[16] = {6'b000000, `gr0, `gr1, `gr3, 5'b00001, 6'b000010}; // srl gr3, gr1, 1 (gr3 <= gr1 >> 1)
uut.instrMemory[17] = {6'b000000, `gr0, `gr1, `gr3, 5'b00001, 6'b000011}; // sra gr3, gr1, 1 (gr3 <= gr1 >>> 1)
uut.instrMemory[18] = {6'b000000, `gr1, `gr2, `gr3, 5'b00000, 6'b000100}; // sllv gr3, gr2, gr1 (gr3 <= gr2 << gr1)
uut.instrMemory[19] = {6'b000000, `gr1, `gr2, `gr3, 5'b00000, 6'b000110}; // srlv gr3, gr2, gr1 (gr3 <= gr2 >> gr1)
uut.instrMemory[21] = {6'b000000, `gr1, `gr2, `gr3, 5'b00000, 6'b101010}; // slt gr3, gr1, gr2 (gr3 <= gr1 < gr2)
uut.instrMemory[26] = {6'b000101, `gr1, `gr2, 16'h0003}; // bne gr0, gr0, 3 (branch 3 if gr1 - gr2 != 0)
uut.instrMemory[30] = {6'b000000, `gr1, `gr2, `gr3, 5'b00000, 6'b100000}; // add gr3, gr1, gr2 (gr3 <= gr1 + gr2)
 uut.instrMemory[31] = \{6'b000010, 26'h000008c\}; \ // \ j \ 0x8c \ (jump \ to \ 0x8c \ unconditionally, \ should \ be \ next \ instruction) 
uut.instrMemory[35] = {6'b000011, 26'h000009c}; // jal 0x9c (jump to 0x9c and link, should be next instruction)
uut.instrMemory[39] = \{6'b000000, gr0, 15'h0000, 6'h8\}; // gr0 (jump to gr0 unconditionally, should start over)
// Initialization
uut.PC = 0;
uut.gr[0] = 0;
clk = 1;
```

#### Intentionally left blank

#### **Output:**

```
| Fetch | Decode |
                                         Memory IO
                      Execute
                                                              Writeback
      : instrD : srcAE : srcBE :ALUOutE: writeDataM:readDataM: resultW: gr1
00000000
00000004:8c010000:xxxxxx
                      xxxxxxxx:xxxxxxx
                                     00000008:8c020004:00000000:00000000:000000000:xxxxxx
0000000c:ac000008:00000000:00000004:00000004: xxxxxxx :0000000ab :xxxxxxxx:xxxxx
00000018:00221820:00000000:00000002:000000002: xxxxxxxx :0000000ab :00000008:000000ab:00003c00:xxxxxxxx
------ Arithmetic Operations ------
0000001c:00221822:000000ab:00003c00:00003cab: xxxxxxxx :0000000ab :00000001:000000ab:000003c00:000000001
00000020:00221821:000000ab:00003c00:ffffc4ab: 00003c00 :xxxxxxxx :00000002:000000ab:00003c00:00000000
00000024:00221823:000000ab:00003c00:00003cab: 00003c00 :xxxxxxxx :00003cab:000000ab:00003c00:00003cab
00000028:00221824:000000ab:00003c00:ffffc4ab: 00003c00 :xxxxxxxx :ffffc4ab:000000ab:00003c00:<mark>ffffc4ab</mark>
0000002c:00221825:000000ab:00003c00:00000000: 00003c00:xxxxxxxx :00003cab:000000ab:000003c00:
00000030:00221827:000000ab:00003c00:00003cab: 00003c00 :000000ab :ffffc4ab:000000ab:000003c00:<mark>ffffc4ab</mark>
00000034:00221826:000000ab:00003c00:ffffc354: 00003c00 :xxxxxxxx :00000000:00000ab:000003c00:
00000038:30031111:000000ab:00003c00:00003cab: 00003cab: 000003cab:000000ab:000003c00: 000003cab
0000003c:34031111:00000000:00001111:00000000: 00003c00 :xxxxxxxx :ffffc354:000000ab:00003c00:<mark>ffffc354</mark>
00000040:00011840:00000000:00001111:00001111: 00003cab:000000ab:000003cab:000000ab:000003c00:
00000044:00011842:000000ab:00000001:00000156: ffffc354 :xxxxxxxx :00000000:000000ab:00003c00:00000000
00000048:00011843:000000ab:00000001:00000055: 000000ab:xxxxxxxx :00001111:000000ab:00003c00:00001111
0000004c:00221804:000000ab:00000001:000000055: 000000ab:xxxxxxxx :00000156:000000ab:00003c00:00000156
00000050:00221806:00003c00:0000000ab:01e00000: 000000ab:xxxxxxxx :000000055:000000ab:000003c00:
00000054:00221807:00003c00:0000000ab:00000007: 00003c00 :xxxxxxxx :000000055:000000ab:000003c00:
```

<u>00000058</u>:0022182a:00003c00:000000ab:00000007: 00003c00 :00003c00 :01e00000:000000ab:000003c00:<mark>01e00000</mark> 0000005c: 1022ffff; 000000ab: 00003c00: 000000001: 00003c00: 000003c00: 00000007: 000000ab: 00003c00: 000000007 00000060:xxxxxxxx:<u>000000ab:00003c00:ffffc4ab</u>: 00003c00 :0000000ab :000000007:0000000ab:00003c00: 00000064:xxxxxxx:xxxxxxxx:xxxxxxx:xxxxxxxx: 00003c00 :xxxxxxxx :00000001:000000ab:00003c00:00000001 00000070:xxxxxxxx:000000ab:00003c00:ffffc4ab|: xxxxxxxx:xxxxxxxx:xxxxxxx:000000ab:00003c00:00000001 00000080: 0800008c: 000000ab: 00003c00: 000003cab: xxxxxxxx : xxxxxxxx : xxxxxxxx: 0000000ab: 00003c00: 000000001 00000084:xxxxxxx:<u>xxxxxxx:xxxxxxx:xxxxxxxx</u>: <u>00003c00:xxxxxxxx</u>:xxxxxxx:000000ab:00003c00:000000001 0000000c:ac000008:00000000:00000004:00000004: 000000ab :xxxxxxx:000000ab:00003c00:00000090

gr1 != gr2

BNE 3

Unconditional

Unconditional

0x9c and link

Unconditional

jump to

gr0 = 0x00

jump to

jump to

0x8c

gr1 != gr2

No BEQ